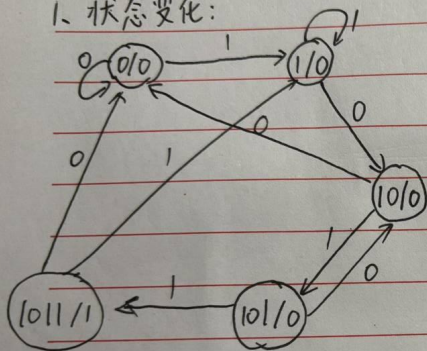





1. 状态变化:




现态	次态		输出
$Q_2 Q_1 Q_0$	$Q_2' Q_1' Q_0'$	Z	
	$X=0$	$X=1$	
0 0 0	0 0 0	0 0 1	0
0 0 1	0 1 0	0 0 1	0
0 1 0	0 0 0	0 1 1	0
0 1 1	0 1 0	1 0 0	0
1 0 0	0 0 0	0 0 1	1

激励函数 $D = Q^{n+1}$
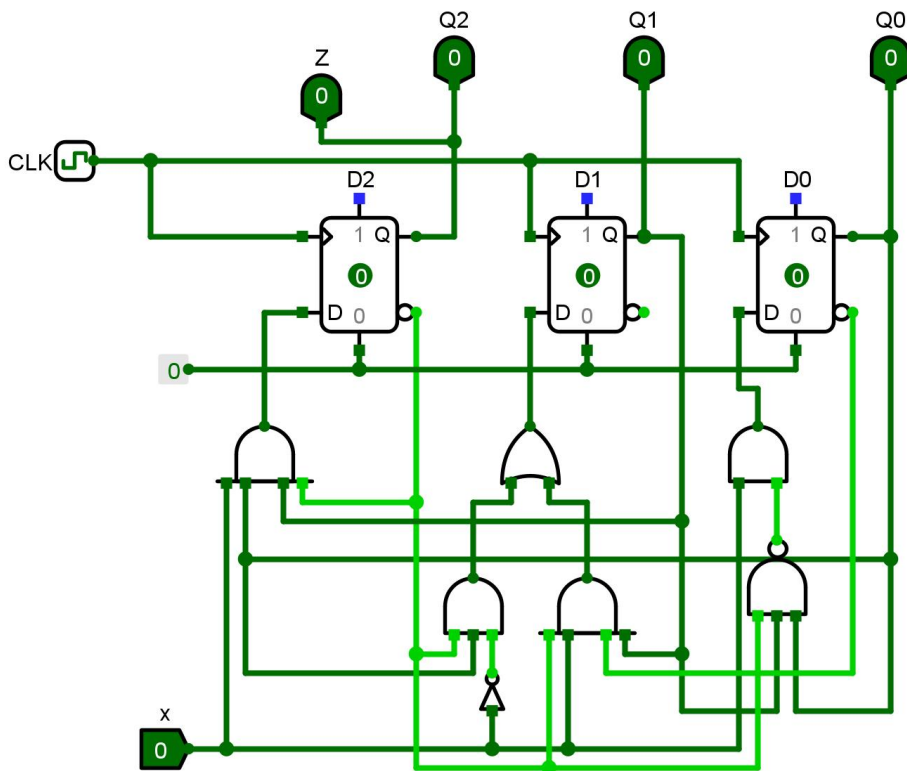
$$D_2 = X \bar{Q}_2 Q_1 Q_0 \quad D_1 = \bar{X} \bar{Q}_2 \bar{Q}_1 Q_0 + \bar{X} \bar{Q}_2 Q_1 Q_0 + X \bar{Q}_2 Q_1 \bar{Q}_0$$
$$D_0 = X \bar{Q}_2 Q_1 \bar{Q}_0 \quad = \bar{X} \bar{Q}_2 Q_0 + X \bar{Q}_2 Q_1 \bar{Q}_0$$
$$Z = Q_2$$



2. 状态变化:

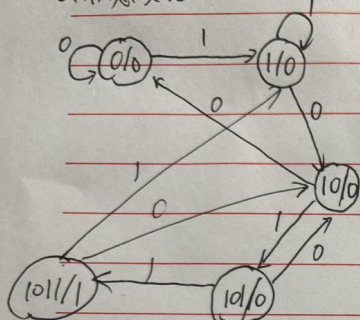

激活函数 $Q_0^{n+1} = J\bar{Q}^n + \bar{K}Q^n$

JK触发器

现态	次态/输出		J_0K_0		J_1K_1	
Q_1Q_0	$x=0$	$x=1$	$x=0$	$x=1$	$x=0$	$x=1$
0 0	0 0 / 0	0 1 / 0	0 d	1 d	0 d	0 d
0 1	1 0 / 0	0 1 / 0	d 1	d 0	1 d	0 d
1 0	0 0 / 0	1 1 / 0	0 d	1 d	d 1	d 0
1 1	1 0 / 0	0 1 / 1	d 1	d 0	d 0	d 1

卡诺图: J_0 :

Q_1Q_0	00	01	10	11
x	0	d	0	d
	1	1	d	1

$J_0 = x$


Q_1Q_0	00	01	10	11
x	d	1	d	1
	1	d	0	d

1701572



华中科技大学附属印刷厂

第 页
 $K_0 = \bar{x}$

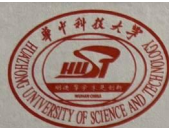

华中科技大学

HUAZHONG UNIVERSITY OF SCIENCE AND TECHNOLOGY
Wuhan 430074, Hubei, P.R.China 中国·武汉 Tel: (027)

Q_1Q_0	00	01	10	11
x	0	1	d	d
	1	0	0	d

$$J_1 = \bar{Q}_1Q_0\bar{x}$$

$$Z = Q_1Q_0x$$

Q_1Q_0	00	01	10	11
x	0	d	1	d
	1	d	d	0

$$K_1 = \bar{Q}_0\bar{x} + Q_0x$$

